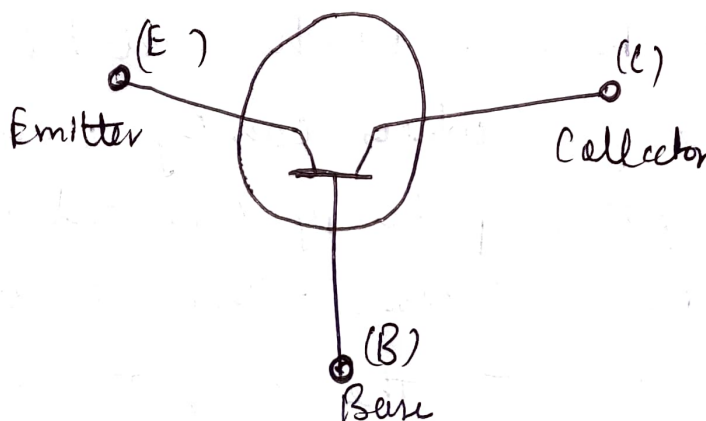


1) Explain the operations of PNP transistor.


The transistor in which one n-type material is sandwiched with two p-type materials such type of transistor is known as PNP transistor.

It is a current controlled device. The small amount of base current controls both the emitter and collector current. The holes are the majority carriers of the PNP transistor which constitute the current in it. This current inside the transistor is constituted because of the changing position of holes and in the leads of the transistor is because of the flow of the electrons. The PNP transistor turns on when a small current flows through the base. The direction of current in PNP transistor is from emitter to collector.


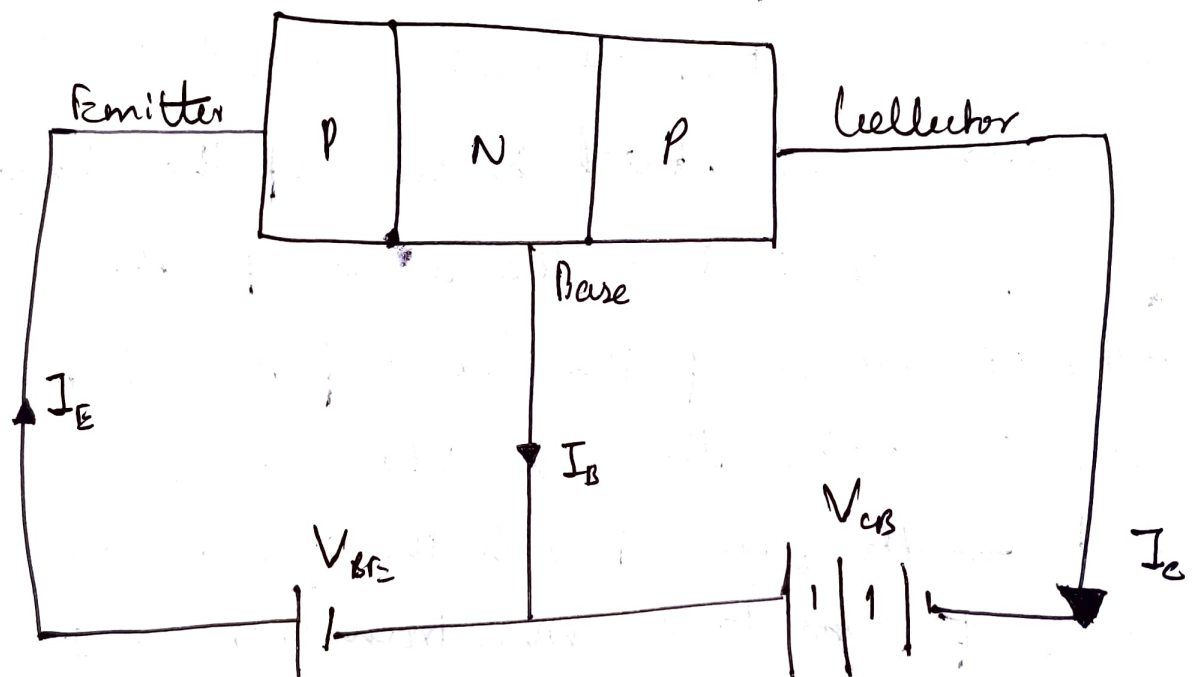
## Working

The emitter base junction is connected in forward biased due to which the emitter pushes the holes in the base region. These holes contribute the emitter current. When these electron move into N-type semiconductor material or base, they combine with the electrons and the remaining are moved towards the collector space charge layer. Hence develops the base current.



The collector base region is connected in reverse biased. The holes which collected around the depletion region when coming under the impact of negative polarity collected or attracted by the collector. This develops the collector current. The complete emitter

current flows through the collector current  $I_c$ .

$$I_E = I_B + I_C$$

$$\alpha = \frac{I_C}{I_E} \quad \beta = \frac{I_C}{I_B}$$

$$\alpha = \frac{\beta}{\beta + 1} \Rightarrow \alpha = \frac{49}{49 + 1} = \frac{49}{50} = 0.8$$


$$I_C = \left( \frac{\beta}{\beta + 1} \right) I_E \Rightarrow I_C = \alpha \cdot I_E = 0.8 \times 3 \text{ mA} \\ = 0.8 \times 3 \times 10^{-3} \text{ A} \\ = 2.4 \text{ mA}$$

③


FET

BJT

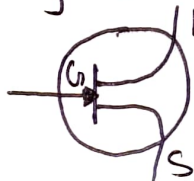
- Field effect transistor
- Has Drain, gate, source terminals
- Classified as N-type or P-type channel
- Conduction only through the majority charge carriers.



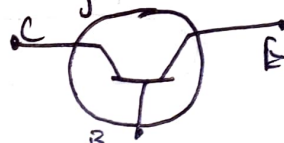
- Bipolar junction transistor
- Has base, emitter, collector terminals
- Classified as NPN, PNP transistor
- Conduction through majority and minority charge carriers



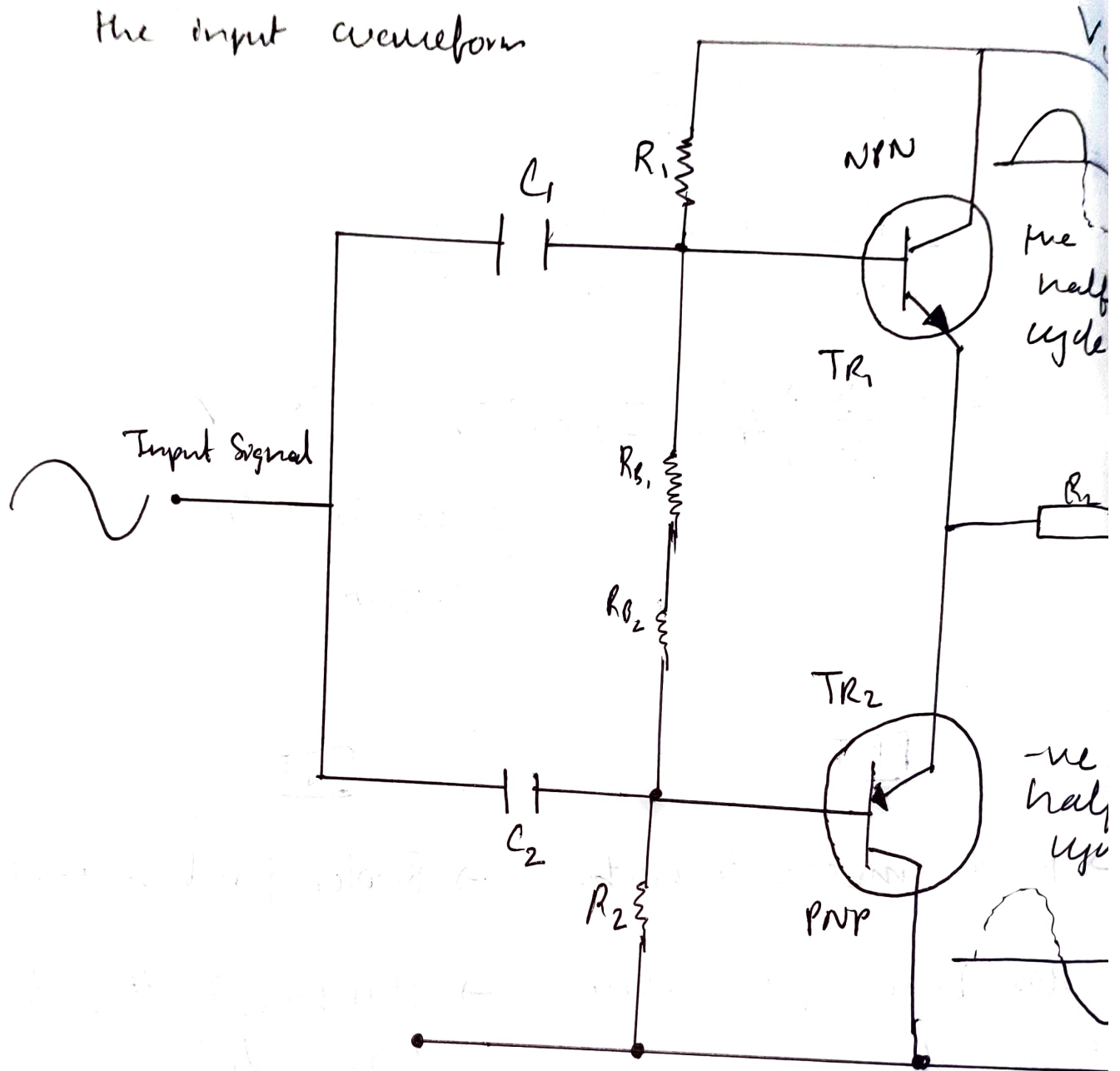- (11) Class B amplifiers use two or more transistors biased in such a way so that each transistor only conducts during one half cycle of the input waveform





### Output Characteristics

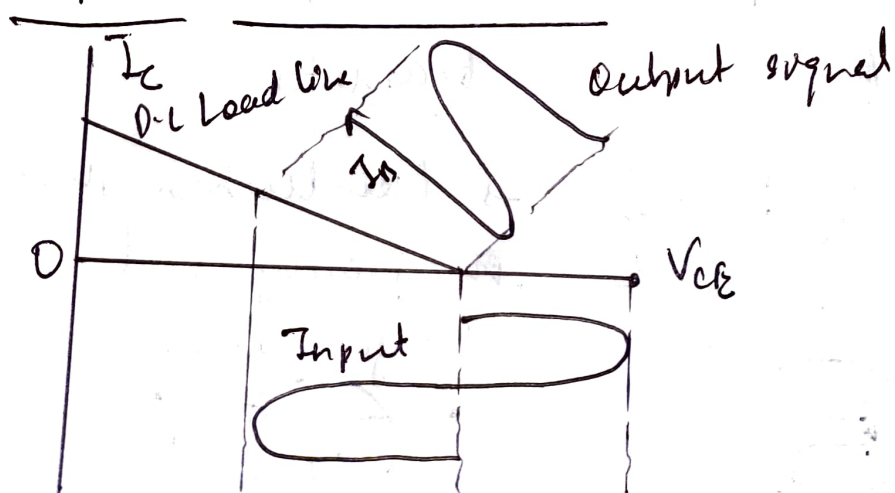



The class B amplifier has a big advantage over the class A amplifier because in that no current flows through the transistors when they are in their quiescent state, therefore no power is dissipated in the output transistors or transformer when there is no signal present unlike class A amplifier.

(5)

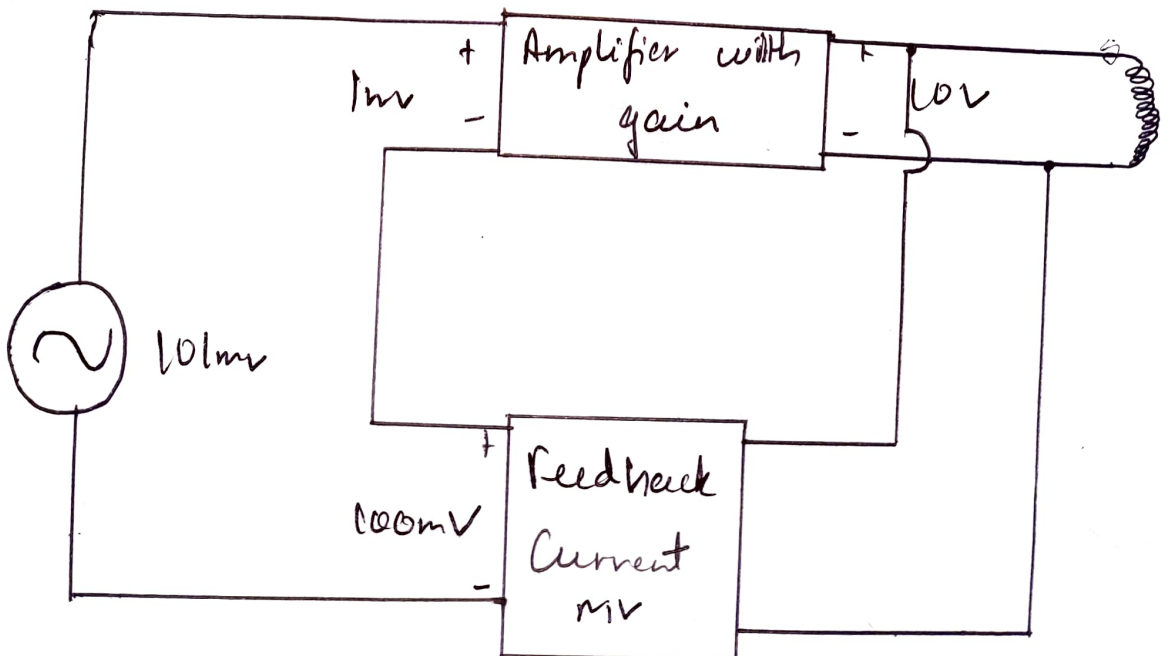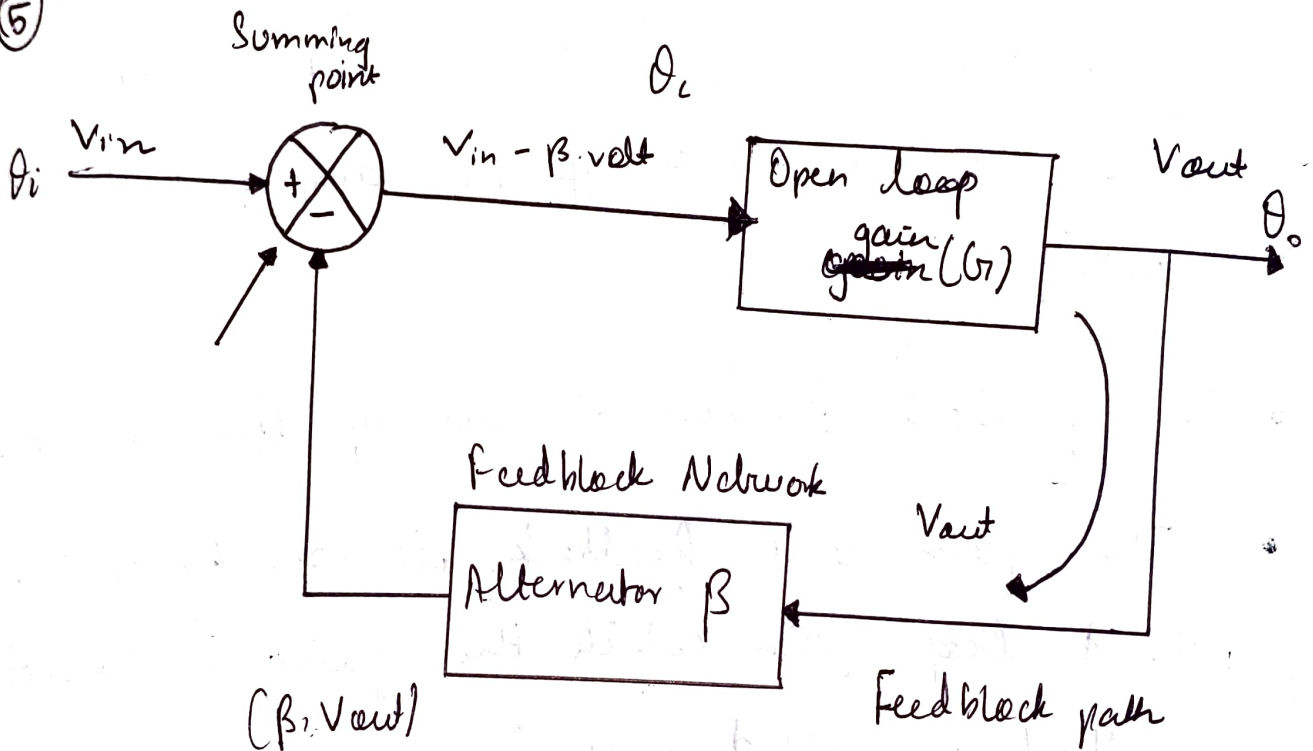

- When negative voltage feedback is applied, the gain of the amplifier is reduced. Thus, the gain of above amplifier without feedback is 10,000 whereas with -ve feedback it is only 100.
- When -ve voltage feedback is applied to the amplifier is ~~exp~~ extremely small. In this case the signal voltage is 101mV and the -ve feedback is 100mV so that voltage applied at the input of the amplifier is only 1mV.
- The feedback fraction is always the  $\frac{1}{100}$ .
- The gain with feedback is sometimes called closed loop gain while the gain without feedback is called open loop gain.